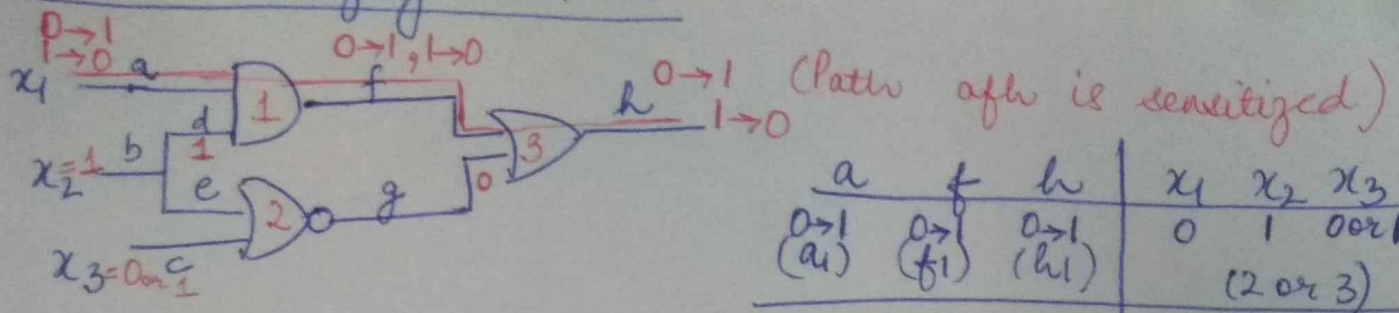


Path sensitizing method:



a	f	h	x ₁	x ₂	x ₃
0→1 (a ₁)	0→1 (f ₁)	0→1 (h ₁)	0	1	0 or 1
					(2 or 3)

① Select a path from primary I/P to primary O/P such that it assigns value of 1 (s-a-0) & 0 (s-a-1) fault to sensitize the path.

② Along chosen path, assign '0' to each I/P of OR & NOR gates and value of '1' to each I/P of AND / NAND gate except the lines of path.

Path: afh \Rightarrow x₁ depends on s-a-0 or s-a-1 fault
 \rightarrow x₂ = 1
 \rightarrow x₃ = 0 or 1.


when x₁ = 1 \Rightarrow O/P = 1 (correct / fault-free ckt)
 if O/P = 0 (ckt has fault of a₀)

when x₁ = 0 \Rightarrow O/P = 0 (correct / fault-free ckt)
 if O/P = 1 (ckt has fault of a₁)

\Rightarrow Test x₁x₂x₃ = 110, 111 (a₀, f₀, h₀)
 010, 011 (a₁, f₁, h₁)

Test 6 or 7 (a₀, f₀, h₀)
 Test 2 or 3 (a₁, f₁, h₁)


Path No.	Path	I/P values to sensitize path	Assigned value of I/P variable of path	Test	Faults detected
1	afh	x ₂ = 1, x ₃ = 0 or 1	x ₁ = 1 x ₁ = 0	6 or 7 2 or 3	a ₀ , f ₀ , h ₀ a ₁ , f ₁ , h ₁
2	bdfh	x ₁ = 1, x ₃ = 0 or 1 x ₁ = 1, x ₃ = 1	x ₂ = 1 x ₂ = 0	6 or 7 5	b ₀ , d ₀ , f ₀ , h ₀ b ₁ , d ₁ , f ₁ , h ₁
3	begh	x ₁ = 0, x ₃ = 0 x ₁ = 0 or 1, x ₃ = 0	x ₂ = 1 x ₂ = 0	2 0 or 4	b ₀ , e ₀ , f ₀ , h ₀ b ₁ , e ₁ , f ₀ , h ₀
4	cgh	x ₁ = 0 or 1, x ₂ = 0 x ₁ = 0 or 1, x ₂ = 0	x ₃ = 1 x ₃ = 0	1 or 5 0 or 4	c ₀ , g ₀ , h ₀ c ₁ , g ₀ , h ₀

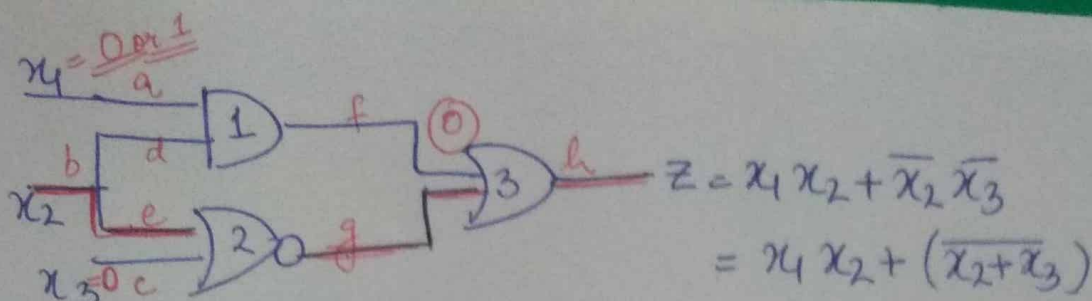

Path b e g h


x_1	x_2	x_3	
1 or 0	0	0	$\Rightarrow b_1, e_1, g_0, h_0$ (0 or 4)
0	1	0	$\Rightarrow b_0, e_0, g_1, h_0$ (2)

b	e	g	h	
0 \rightarrow 1	0 \rightarrow 1	1 \rightarrow 0	1 \rightarrow 0	(Path is sensitized)
1 \rightarrow 0	1 \rightarrow 0	0 \rightarrow 1	0 \rightarrow 1	
b_1	e_1	g_0	h_0	
b_0	e_0	g_1	h_1	

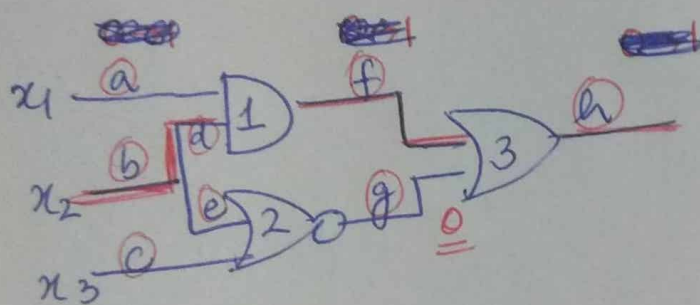


b	d	f	h	$x_1 x_2 x_3$
0 \rightarrow 1	0 \rightarrow 1	0 \rightarrow 1	0 \rightarrow 1	0 0 0
(b_1)	(d_1)	(f_1)	(g_1)	1 0 1 (5)
1 \rightarrow 0	1 \rightarrow 0	1 \rightarrow 0	1 \rightarrow 0	1 1 0 (6)
(b_0)	(d_0)	(f_0)	(g_0)	1 1 1 (7)

Path b d f h

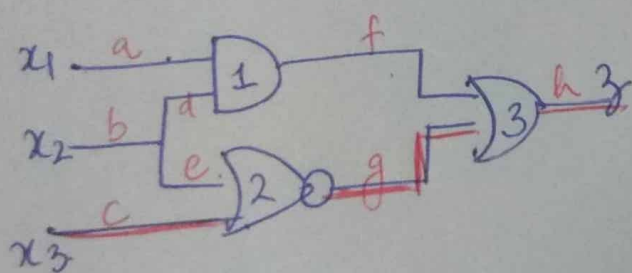

Path c g h

c	g	h	$x_1 x_2 x_3$
0 \rightarrow 1	1 \rightarrow 0	1 \rightarrow 0	0 0 0 (0)
(c_1)	(g_0)	(h_0)	1 0 0 (4)
1 \rightarrow 0	0 \rightarrow 1	0 \rightarrow 1	0 0 1 (1)
(c_0)	(g_1)	(h_1)	0 0 0
			1 0 1 (5)

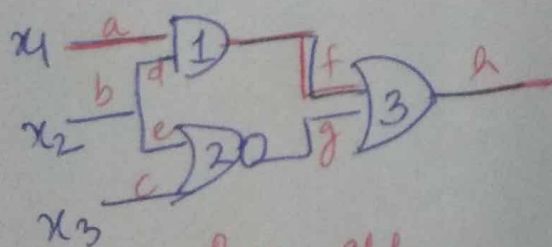

Path a f h

a	f	h	$x_1 x_2 x_3$
0 \rightarrow 1	0 \rightarrow 1	0 \rightarrow 1	0 1 0 (2)
(a_1)	(f_1)	(h_1)	0 1 1 (3)
1 \rightarrow 0	1 \rightarrow 0	1 \rightarrow 0	1 1 0 (6)
(a_0)	(f_0)	(h_0)	1 1 1 (7)