

Q-M for multi-output fns:-

①

- Identify the PI for individual outputs and for their products.

eg: 2 fns: $f_1, f_2 \Rightarrow$ PI for $f_1, f_2, f_1 \cdot f_2$

3 fns: $f_1, f_2, f_3 \Rightarrow$ PI for $f_1, f_2, f_3, f_1 \cdot f_2, f_1 \cdot f_3, f_2 \cdot f_3$ and $f_1 \cdot f_2 \cdot f_3$.

- Obtain Augmented PI chart & identify Essential PI for individual fns. Then use dominated/dominating rows/cols or branching method to reduce the table if needed (If objective is to minimize the no. of gates in multi-outputs ckt implementation).
- If secondary objective is to minimize the interconnections, then removing dominated rows is not allowed as it may eliminate solⁿ which has fewer interconnections.

considers 2 fns f_1 & f_2 . Use QM method to implement ckt.

$$f_1 = \sum m(2, 6, 7)$$

$$f_2 = \sum m(1, 2, 3)$$

$x \backslash yz$	00	01	11	10
0	0	1	3	2
1	4	5	7	6

$$f_1 = xy + y\bar{z}$$

$x \backslash yz$	00	01	11	10
0	0	1	3	2
1	4	5	7	6

$$f_2 = \bar{x}y + \bar{x}z$$

$x \backslash yz$	00	01	11	10
0	0	1	3	2
1	4	5	7	6

$$f_1 \cdot f_2 = \bar{x}y\bar{z}$$

Augmented PI chart:


f_n	PI	f_1			f_2		
		2	6	7	1	2	3
f_1	$A = xy$ $B = y\bar{z}$		X	X			
f_2	$C = \bar{x}y$ $D = \bar{x}z$	X	X			X	X
$f_1 \cdot f_2$	$E = \bar{x}y\bar{z}$	X				X	

A & D are Essential PI.

Reduced PI chart:

f_n	PI	f_1	f_2
f_1	$B = y\bar{z}$	X	
f_2	$C = \bar{x}y$		X
$f_1 \cdot f_2$	$E = \bar{x}y\bar{z}$	X	X

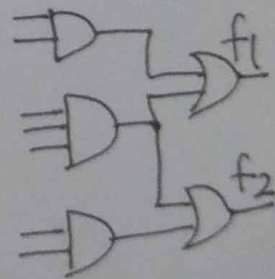\therefore ckt will have 3 terms $xy, \bar{x}z$ and $\bar{x}y\bar{z}$



Multiple switching for minimization criterion:

- ① Each minimized fn should have as many terms in common with those in other minimized fns as possible.
 - ② Each fn should have min. no. of product terms (SOP) or sum terms (for POS).
- use single PI table (Augmented PI chart) by considering all fns together, using a term Tag.

$f_1(x_1, x_2, x_3, x_4) = \sum m(1, 2, 3, 5, 7, 8, 9, 12, 14)$
 $f_2(x_1, x_2, x_3, x_4) = \sum m(0, 1, 2, 3, 4, 6, 8, 9, 10, 11)$
 $f_3(x_1, x_2, x_3, x_4) = \sum m(1, 3, 5, 7, 8, 9, 12, 13, 14, 15)$

<u>Index</u>	<u>Decimal no.</u>	<u>Binary</u>	<u>f1</u>	<u>f2</u>	<u>f3</u>	
0	0	0000	0	1	0	✓
	1	0001	1	1	1	✓
	2	0010	1	1	0	✓
	4	0100	0	1	0	✓
	8	1000	1	1	1	✓
2	3	0011	1	1	1	✓
	5	0101	1	0	1	✓
	6	0110	0	1	0	✓
	7	0111				
	9	1001		1	1	✓
	10	1010		0	1	✓
	12	1100		1	0	✓
	7	0111	1	0	1	✓
	11	1011	0	1	0	✓
	13	1101	0	0	1	✓
3	14	1110	1	0	1	✓
	15	1111	0	0	1	✓

Tag

Decimal nos	First Reduction	f1 f2 f3
0,1 (1)	0 0 0 -	0 1 0 ✓
0,2 (2)	0 0 - 0	0 1 0 ✓
0,4 (4)	0 - 0 0	0 1 0
0,8 (8)	- 0 0 0	0 1 0 ✓
1,3 (2)	0 0 - 1	1 1 1 A
1,5 (4)	0 - 0 1	1 0 1 ✓
1,9 (8)	- 0 0 1	1 1 1 B ⇒
2,3 (1)	0 0 1 -	1 1 0 C
2,6 (4)	0 - 1 0	0 1 0 ✓
2,10 (8)	- 0 1 0	1 0 0 ✓
4,5 (1)	0 1 0 -	0 0 0
4,6 (2)	0 1 - 0	0 1 0 ✓
4,12 (8)	- 1 0 0	0 0 0
8,9 (1)	1 0 0 -	1 1 1 D
8,10 (2)	1 0 - 0	0 1 0 ✓
8,12 (4)	1 - 0 0	1 0 1 E
3,7 (4)	0 - 1 1	1 0 1 ✓
3,11 (8)	- 0 1 1	0 1 0 ✓
5,7 (2)	0 1 - 1	1 0 1 ✓
5,11 (8)	0 1 1 -	0 0 0
5,13 (8)	- 1 0 1	0 0 1 ✓
6,7 (1)	0 1 1 -	0 0 0
6,14 (8)	- 1 1 0	0 0 0
9,11 (2)	1 0 - 1	0 1 0 ✓
9,13 (4)	1 - 0 1	0 0 1 ✓
10,11 (1)	1 0 1 -	0 1 0 ✓
10,14 (4)	1 - 1 0	0 0 0
12,13 (1)	1 1 0 -	0 0 1 ✓
12,14 (2)	1 1 - 0	1 0 1 F
7,15 (8)	- 1 1 1	0 0 1 ✓
11,15 (4)	1 - 1 1	0 0 0
13,15 (2)	1 1 - 1	0 0 1 ✓
14,15 (1)	1 1 1 -	0 0 1 ✓

Quads	f1 f2 f3
0,1,2,3 (1,2)	✓ 0 1 0
0,1,8,9 (1,8)	✓ 0 1 0
0,2,4,6 (2,4)	G 0 1 0
0,2,8,10 (2,8)	✓ 0 1 0
1,3,5,7 (2,4)	H 1 0 1
1,3,9,11 (2,8)	✓ 0 1 0
1,5,9,13 (4,8)	I 0 0 1
2,3,10,11 (1,8)	✓ 0 1 0
8,9,10,11 (1,2)	✓ 0 1 0
8,9,12,13 (1,4)	J 0 0 1
5,7,13,15 (2,8)	K 0 0 1
12,13,14,15 (1,2)	L 0 0 1

Tag.

Octet
0,1,2,3,8,9,10,11
(1,2,8) M

Tag
f1 f2 f3
0 1 0

PI are
A, B, C, D, E,
F, G, H, I, J,
K, L, M.

Red groups doesn't exist for any fn. so they are not considered for next reduction.

Tag

		f_3	
		14	15
LDF	F	X	
LJK	K		X
	L	X	X

$$f_1 = C + D + F + H$$

$$f_2 = G + M$$

$$f_3 = D + H + L$$

	1	2	3	5	7	8	9	12	14	0	1	2	3	4	6	8	9	10	11	12	3	5	7	8	9	12	13	14	15			
A	X		X								X		X							X	X										H2A	
B	X						X				X						X			X						X					D2B	
C		(X)	X									X	X																			
D							X	X								(X)	X								X	X					D2E	
E							X		X																X		X					
F								X	X																		X		X			
G										(X)	X		(X)	(X)																		
H	X		X	X	X															X	X	X	X									
I																				X		X			X		X				D2Z	
J																									X	X	X	X				D2J
K																						X	X				X		X			
L																											X	X	X	X		
M										X	X	X	X		X	X	X	X	X													
	127		322	507					12714	026	1211	226	3211	4=6	8211	9211	10211	123		527							12714	13715				Remove A, B, E, I, J